

## 5.1 Electric fields

### Equations

- Current - charge relationship:  $I = \frac{dq}{dt}$
- Coulomb's law:  $F = k \frac{q_1 q_2}{r^2}$
- The coulomb constant:  $k = \frac{1}{4\pi\epsilon_0}$
- Potential difference definition:  $V = \frac{W}{q}$
- Conversion of energy in joules to electron volts:  $1 \text{ eV} = 1.6 \times 10^{-19} \text{ J}$
- Electric field strength:  $E = \frac{F}{q}$
- Drift speed:  $I = nAvq$

### Combining electrostatics

- Positively charged objects are attracted to negative ones.
- There can also be an attraction between an uncharged and charged object due to the separation of charge in the uncharged object.
  - In the example with figures 1C the electron are attracted to charged sphere B.
  - This is because of the fact that the charged particles from the charged sphere will be attracted to the opposite charges on the neutral sphere.
  - If the sphere get closer to one another the forces increase.

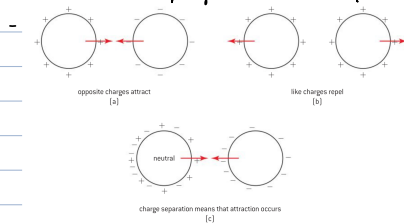


Figure 1 Attractions between charges.

- An object with an exact balance of electrons and protons will be found to be neutral.
  - In conducting material the electrons are detached, therefore the material can be positively charged.
- Charge is conserved: In a closed system the amount of charge is constant.
- The following figure will show how to charge a sphere through induction:

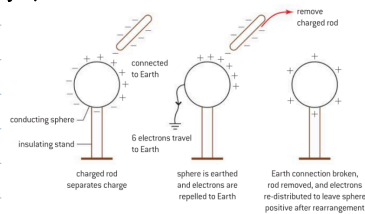


Figure 2 Charging by induction.

### Measuring and Defining Charge

- Charge is in coulombs (C).
  - It's a scalar quantity.
  - The coulomb is defined as the charge transported by a current of one ampere in one second.
- Electron will have a charge of  $-1.6 \times 10^{-19} \text{ C}$ , this amount is known as the elementary charge.
  - Elementary charge has the symbol " $e$ ".
  - Proton will have a fractional charge which appear as  $\pm \frac{1}{3}e$  or  $\pm \frac{2}{3}e$ .

### Force between charged objects

- The force between two small point charges separated by distance " $r$ " is proportional to:  $\frac{1}{r^2}$ .
  - This is an inverse-square law.
- The magnitude of the force  $F$  is between two point charges of charge  $q_1$  and  $q_2$  separated by distance  $r$  in a vacuum is given by:
 
$$F = k \frac{q_1 q_2}{r^2}$$
  - where  $k$  is the coulomb constant.
- The coulomb constant is given by:  $k = \frac{1}{4\pi\epsilon_0}$ , where " $\epsilon_0$ " is the permittivity of free space.
- In the case of the force not occurring in a vacuum the  $\epsilon_0$  will change to  $\epsilon$ .
- The direction of the force will come by the equation  $F = q_1 E_2$ .

Therefore, the direction left to right will be assigned the positive direction.

**Worked example**

$$F = \frac{(1.0 \times 10^{-9})^2}{15 \times 10^{-11}}$$

$$= 4.0 \times 10^{-9} \text{ N}$$

$$F = \frac{(5 \times 10^{-9})(5 \times 10^{-9})}{6 \times (8.85 \times 10^{-12}) \times 1.5^2}$$


$$= 2.5 \times 10^{-9} \text{ N}$$

**Electric field**

- the term field is used in physics when two separate objects exert forces on each other.
- E.g. comb picking up paper, the paper is in the electric field due to the comb.

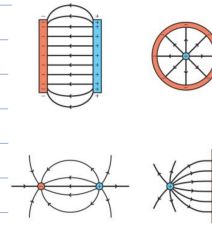**Mapping fields**


- there are some conventions for drawing their electric field patterns:
  - the lines start and end on charges of opposite signs.
  - the arrows is essential to show the direction in which a positive charge would move.
  - therefore the arrows will go from the positive charge to the negative one.
  - the field is strongest where the lines are close together.
  - the lines act to repel one another.
  - the lines never cross.
  - the lines will meet a conducting surface at 90°.



▲ Figure 8 Electric field patterns.

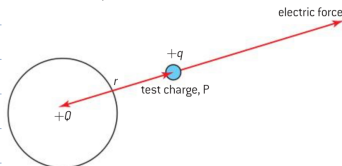
**Electric field strength**

- the electric field strength is defined using the concept of a positive test charge.
- imagine an isolated charge Q sitting in space. To know the field strength at point P at distance r away from the isolated charge, we put another positive test charge of size q at point P, to measure force F.
- the magnitude of the electric field strength is defined to be:  $E = \frac{F}{q}$ .



▲ Figure 9 Definition of electric field strength.

- the units of the electric field strength are  $\text{N C}^{-1}$ .
- electric field strength is a vector, it has some direction or the force F.
- the formal definition of electric field strength at a point: the force per unit charge experienced by a small positive point charge placed at that point.
  - Q is the isolated point charge, and q is the test charge.
  - therefore,  $E = \frac{F}{q}$ .
  - the electric field strength of the charge at a point is proportional to the charge, and inversely proportional to the distance from the charge.
  - if Q is positive, then E is also positive.
    - when the point charge is positive, the field lines will be pointing out.
    - when the point charge is negative, the field lines will point in.
- the field shape for a point charge is known as a radial field.

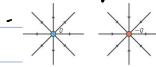

▲ Figure 10 Radial fields for positive and negative point charges.


**Worked example**

$$E = \frac{kq}{r^2} = \frac{(9 \times 10^9)(1.0 \times 10^{-9})}{1.5^2} = 4.0 \times 10^9 \text{ N C}^{-1}$$

$$E = \frac{kq}{r^2} = \frac{(9 \times 10^9)(5 \times 10^{-9})}{1.5^2} = 2.0 \times 10^9 \text{ N C}^{-1}$$

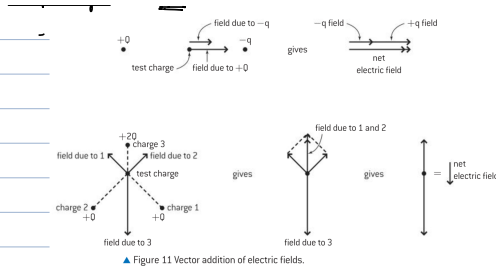- the electric field strengths can be added.





**Close to conductor**

- what occurs near the surface of a conductor is:


- when you're close enough to a surface, it will appear to be flat.

- the electrons are equally spaced.

- this is because of the fact that all electrons near the surface will equally push one another away causing a state of equilibrium.

- any force which is parallel to the surface will be cancelled out.

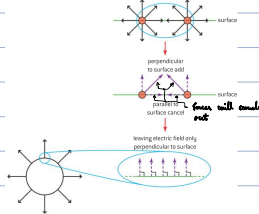- perpendicular to the surface the field vectors will add up.



**conducting spheres**

- for a conducting sphere the radial field will look exactly the same as a point charge.

- inside the sphere there is no electric field, hollow or solid. - the total charge is equal to the total charge spread over the sphere.

**worked example**

- the resultant electric field strength when point charges of  $4 \mu\text{C}$  and  $9 \mu\text{C}$  is

$$E_1 = \frac{kq}{d^2} = \frac{9 \times 10^9 (4 \times 10^{-6})}{(0.05)^2} = 1.44 \times 10^8 \text{ N/C}$$

$$E_2 = \frac{kq}{d^2} = \frac{9 \times 10^9 (9 \times 10^{-6})}{(0.05)^2} = 3.24 \times 10^8 \text{ N/C}$$

$$E = 3600 - 7200 = 1400 \text{ N/C towards } q_2$$

- the distance for the electric field to be zero is:

$$E_{net} = -E_1$$


$$\frac{(9 \times 10^9)q}{d^2} = \frac{(9 \times 10^9)Q}{(0.5-d)^2}$$

$$\frac{d}{(0.5-d)} = \sqrt{\frac{Q}{q}}$$


$$d = 0.05 - 1.5d$$

$$d = \frac{0.05}{2.5}$$

$$d = 0.02 \text{ m}$$

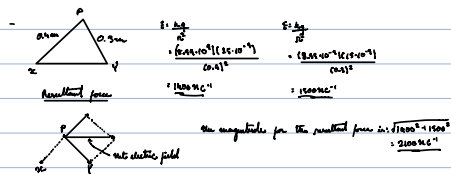

**Measuring charges**

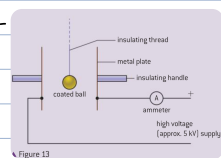

- When a current is supplied to the circuit, an excess of electrons will appear on the plate which is connected to the negative supply.
  - The other plate will have a deficit of electrons making it positive.
- When the ball touches one of the plates, it will either gain or lose electrons.
  - When it touches the negatively charged plate, electrons will flow into the ball causing it to become negatively charged.
    - This will then mean that the ball is repelled by the negative plate, and be attracted to the positively charged one.
  - Once the ball arrives at the positive side, it will transfer its electrons to the positive side, causing it to become positively charged, resulting in it being repelled by the positive end, and attracted to the negative side.
- Whilst the ammeter shows that there is a flow of electrons going clockwise that:
  - The electric current results when charges move.
  - The charge is caused by the presence of an electric field.

### - Mechanism for electric current

- Electrical conduction is possible in gases, liquids, solids, and a vacuum.

### - Conduction metals

- Metal atoms in a solid are bound together by metallic bonds.
- In a metal, the atoms are arranged into a lattice, and their electrons are delocalised.
  - This means that the electrons aren't bound to a single atom, and therefore, will be able to conduct electricity.

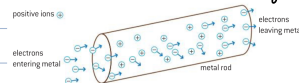


Figure 14 Conduction by free electrons in a metal.

- The positive ions sit in fixed positions on the lattice.
  - There are ions on each lattice site because each atom has lost an electron.
- There is still interaction between the electrons and atoms.
  - The electrons will collide with the vibrating ions and transfer kinetic energy.

### - This is resistance

- The energy transfer is:

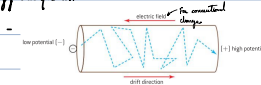


Figure 15

- In a metal, the electrons will be travelling at random and average speed, which are close to the speed of sound in the material.
  - This is without an electric field being present.
- When an electric field is present, then an electrical force will act on the electrons with their negative charge.
  - The force of electrons will be in the opposite direction of the electric field, as the electric field is for conventional charge.
  - The electrons will drift along the conductors.
    - They're known as charge carriers.
    - Their movement is in a random direction.

### - Conduction in gases and liquids

- Electrical conduction will occur in other materials as well.
  - Most gas and liquid will contain ions.
    - The ions will then become the charge carriers.
    - Causing a current.
    - Positive in the direction of the field, and negative the opposite way.
  - If the electric field is strong enough, then ions in the gas are formed, leading to a phenomenon known as dielectric breakdown.
    - E.g. lightning during a storm.

### - Electric current

- It's a current is charge flowing in a conductor.
  - Measured in Amperes, or amps (A).

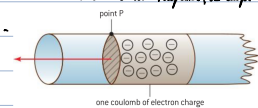


Figure 16 Charge flow leading to current.

- One ampere (amp) can be defined as the number of electrons that pass a certain point per second.

- Mathematically current is given by: electric current,  $I = \frac{\text{total charge passing point in point}}{\text{time taken for charge to pass point}}$   $\rightarrow I = \frac{Q}{t}$

- Worked example

-  $f = 0.67 \text{ Hz}$ ,  $q = 72 \text{ nC}$

$$\bar{I} = \frac{72 \cdot 10^{-9}}{0.75} \quad I = \frac{1}{f} = 0.75 \text{ A}$$

$$= 9.6 \cdot 10^{-9} \text{ Amps}$$

-  $4.5 \cdot 10^{11}$  electrons

-  $I = 9.6 \cdot 10^{-9} \text{ A}$ ,  $t = 60 \text{ s}$

$$I = \frac{q}{t}$$

$$q = \frac{I \cdot t}{1}$$


$$= 5.76 \text{ C}$$

- Charge carrier drift speed

- The slow speed at which the ions move along the conductor is known as the drift speed.

- For a conductor with a current  $I$ , cross-sectional area  $A$ , containing charge carriers with charge  $q$ .

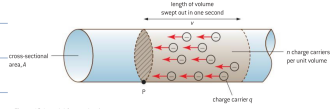- We assume that each charge carrier will have a speed  $v$ , and that there are  $n$  charge carriers in  $(\text{m}^3)$  of conduction known as charge density.



- In one second, a volume  $Av$  of charge carriers passes  $P$ .

- The total number of charge carriers in this volume is  $nAv$  and therefore the total charge in the volume is  $nAvq$ .

- The current  $I$  therefore given by:  $I = nAvq$ .

- Standard example

- diameter =  $0.65 \cdot 10^{-3} \text{ m}$ ,  $I = 0.35 \text{ A}$ ,  $n = 9.5 \cdot 10^{28}$ ,  $q = 1.6 \cdot 10^{-19} \text{ C}$

$$I = nAvq \quad v = \frac{I}{nAq}$$

$$= \frac{0.35}{(9.5 \cdot 10^{28}) \cdot (\frac{0.65 \cdot 10^{-3}}{2})^2 \cdot (1.6 \cdot 10^{-19})}$$

$$= 5.91 \cdot 10^{-9} \text{ m s}^{-1}$$

- The reason that this drift velocity is so small is because of the fact that there are many free electrons available for conduction in the metal.

- Even though the electrons move at such a slow speed, the information of them being to move travels through the conductor at nearly the speed of light, meaning that it will be able to turn on appliances instantly.

- Potential difference


- Potential difference (pd) is a measure of the electrical potential energy transferred from one electron when its moving between two points.

- The potential difference is defined by the work done (energy transferred)  $W$  when one unit of charge  $Q$  moves between two points.

- This is given by the equation: pd (V) =  $\frac{W}{Q}$ .

- The units for potential are  $\text{J C}^{-1}$  or V (volts).

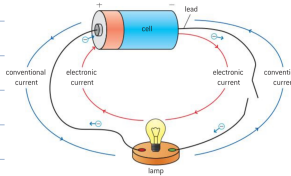- The potential difference between two points is one volt if one joule of energy is transferred per coulomb of charge passing between the two points.



- When the switch is closed, electrons will flow through the circuit.

- Conventional current will be in the opposite direction of the actual current.

- The actual current (how electrons will flow in the circuit), will go from the negative electrode (cath) to the positive electrode of the cell/battery.

- The conventional current will be going from the positive electrode to the negative.

- In the electron moves around the circuit they will gain electric potential energy as it moves through the cell.

- The electrons will lose all the electric potential energy which they gained at the cell.

- The electrical potential energy is used to do work when the electrons move through the lamp.

- Lamps (resistors) are designed so that as much electrical potential energy is caused from the electrons.

- The electrical potential energy transferred by the electrons to the atoms in the lamp will mean that the atoms in the lamp will vibrate with greater amplitude and speed, resulting in the filament heating to glow.
- Therefore, the pd across the lamp will be high due to the fact that a lot of the electron energy is being transferred to the atoms in the resistor.

Worked example

$V = 240 \text{ V}$ ,  $I = 50 \text{ mA} = 50 \times 10^{-3} \text{ A}$ ,  $t = 7500 \text{ s}$   
 $Q = I \Delta t = (50 \times 10^{-3})(7500) = 375 \text{ C}$   
 Energy transferred  $W = UQ = (240)(375) = 90000 \text{ J}$   
 $V = IR$ ,  $R = 480 \Omega$   
 $W = I^2 R t = (0.05)^2 (480) (7500) = 1125 \text{ J}$   
 $I = 50 \text{ mA}$ ,  $Q = I \Delta t$   
 $\Delta t = \frac{Q}{I} = \frac{375}{0.05} = 7500 \text{ s}$

Electromotive force

- Electromotive force isn't a force, but instead is used when energy is transferred to the electrons in a battery (eg).

Device	converts energy from	into	pd or emf?
Cell	chemical	electrical	emf
Resistor	electrical	internal	pd
Microphone	sound	electrical	emf
Loudspeaker	electrical	sound	emf
Lamp	electrical	light (and internal)	pd
Photovoltaic cell	light	electrical	emf
Dynamo	kinetic	electrical	emf
Electric motor	electrical	kinetic	pd

Resistors do work resulting in them losing energy, and therefore a pd acrossing.

Power, current, and pd

- In time  $\Delta t$ , the charge  $Q$  that moves through the conductor is equal to  $I \Delta t$ .
- The energy transferred in time  $\Delta t$  is:  $W = U I \Delta t$
- Electrical power is given by:  $P = UI$
- The units of power is watt, W.

Worked example

$V = 1.5 \text{ V}$ ,  $P = 0.5 \text{ W}$   
 $P = UI$ ,  $I = \frac{P}{U} = \frac{0.5}{1.5} = 0.33 \text{ A}$   
 $W = I^2 R t$ ,  $R = 1.5 \Omega$ ,  $t = 70 \text{ s}$ , efficiency  $0.4$   
 $E = 40 \text{ Ah}$ ,  $U = 1.5 \text{ V}$ ,  $W = I U t = 0.33 \times 1.5 \times 70 = 3.5 \text{ Wh}$   
 $E = 40 \text{ Ah} \times 1.5 \text{ V} = 60 \text{ Wh}$   
 $\text{Efficiency} = \frac{3.5}{60} = 0.058$

The electronvolt

- If a single electron moves through a potential difference of 1V, then the energy transferred to the electron will be  $(1.6 \times 10^{-19} \text{ C}) \times 1 \text{ V} = 1.6 \times 10^{-19} \text{ J}$ .
- Hence the value is so small, it is more convenient to use the unit "electronvolt" (eV).
- 1 electronvolt will be equal to  $1.6 \times 10^{-19} \text{ J}$ .

Worked example

$U = 190 \text{ V}$ ,  $W = 1.6 \times 10^{-19} \text{ J}$   
 $Q = \frac{W}{U} = \frac{1.6 \times 10^{-19}}{190} = 8.4 \times 10^{-22} \text{ C}$   
 $n = \frac{Q}{e} = \frac{8.4 \times 10^{-22}}{1.6 \times 10^{-19}} = 5.25 \times 10^{-4}$   
 $A = 550 \text{ A}$   
 $W = I U t$ ,  $t = \frac{W}{I U} = \frac{1.6 \times 10^{-19}}{550 \times 190} = 1.5 \times 10^{-22} \text{ s}$

3.2 Heating effect of an electric current

Equations

- Resistance definition:  $R = \frac{U}{I}$
- Electrical power:  $P = UI = I^2 R = \frac{U^2}{R}$
- Combining resistors in series:  $R_{\text{total}} = R_1 + R_2 + R_3 + \dots$
- Combining resistors in parallel:  $\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$
- Resistance definition:  $\rho = \frac{R A}{L}$

Effect of electric current

- Effect that occur when charge flows through a circuit.
  - Heating effect: when energy is transferred to a resistor or internal energy
  - Chemical effect: when chemicals react together to alter the energy of electrons and cause them, when electric current in a material cause chemical change
  - Magnetic effect: when a current produces a magnetic field, when magnetic field change near conductor and induces an e.m.f in the conductor.

Drawing and using circuit diagrams

Circuit symbols

joined wires	wires crossing (not joined)	coil

- Some symbols are reserved for direct current (d.c.), such as cells and batteries.
  - Direct current is where the charge will flow in one direction.
  - E.g. planes and low-voltage pluglights.
- Other electrical circuits will use alternating current (a.c.).
  - This is where the current will alternate in its direction.
  - The time between the change is usually  $\frac{1}{50}$  of a second.
  - This type of current is used for high power devices.
- The difference between a cell and a battery is that a battery will be an arrangement of cells, arranged by having positive terminal to negative.

Circuit connections

- Write values with symbol of the object.
- If two wires are connected at one point, then a joint is placed where they connect.
  - This joint is called a junction.

Resistance

- As a current passes through a wire it will heat up due to the fact that the electrons will constantly interact with the wire atoms causing them to gain kinetic energy, causing them to vibrate at greater speeds, and greater amplitudes.
  - This is what causes resistance in wires.
  - Different wires will have different resistance values, e.g. at the same wire length, one will have a greater temperature rise than copper.
- Resistance is defined as:  $\frac{\text{potential difference across component}}{\text{current in the component}} \rightarrow R = \frac{V}{I}$ .
  - Units are Ohms ( $\Omega$ ).

Ohm's law

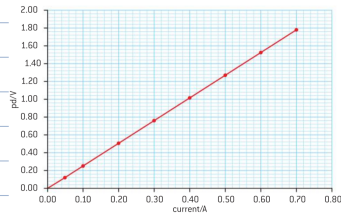


Figure 6 pd against current from the table.

- When the resistance will increase by the same value, then the resistor is said to be Ohmic.
  - Meaning  $V \propto I$
- Ohm's law states that the potential difference across a suitable conductor is directly proportional to the current in the conductor.
  - This is the case if the physical properties are the same.
  - This means that the temperature and other variables.
- If the resistance will not increase on a straight line when it's plotted, meaning  $V$  is not proportional to  $I$ , then the resistor will be non-ohmic.
  - E.g. filament bulb.

• this can be done to varying temperatures.

Resistivity:

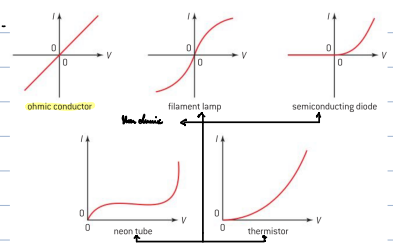


Figure 8 - V graphs for various conductors.

Resistivity diode

- these are designed to have current only flow in one direction
- symbol:  $\begin{array}{|c|} \hline \text{D} \\ \hline \end{array}$

Resistor

- there are made of one two element that are electrical resistors: silicon and germanium.
- the negative temperature coefficient thermistor is designed that when the temperature of the wire thermistor increases, its resistance falls.
  - the opposite that occurs in metals
- Resistor have fewer free electron per cubic meter compared with metals.
  - their resistance is usually 10<sup>3</sup> times greater than
  - the charge density strongly depend on Temp.
    - the higher the temperature, the more charge carriers are available
- In the Temp of germanium increases:
  - the lattice will vibrate more causing the movement of charge carrier.
    - leading to an increase in resistance cause an unstable
  - as the temperature increases, there more charge carrier would become available.
    - leading to resistance falling
    - this effect will be greater than the first, meaning that as Temp increases, the resistance will fall.

Resistivity

- the size and shape of a material will also affect its resistance.
  - the resistance of a conductor is:
    - proportional to its length  $l$ .
    - inversely proportional to its cross-sectional area  $A$  (which is proportional to  $d^2$ ).
      - $R \propto \frac{l}{A}$
  - this leads to a definition of a new quantity called resistivity ( $\rho$ ):
    - $\rho = \frac{RA}{l}$
    - the units are  $\Omega \cdot m$ .

Worked example:

- A  $0.16 \cdot 10^{-3} m$ ,  $1.75 mm$ ,  $\rho = 7 \cdot 10^{-8} \Omega m$

$$\frac{\rho l}{A} = R \quad R \propto \frac{l}{A}$$

$$R = 65 \Omega \quad \frac{7 \cdot 10^{-8} \cdot 1.75 \cdot 10^{-3}}{2 \cdot 10^{-6}}$$

-  $1 \cdot 0.025 m$ , width =  $0.75 mm$ , thickness =  $13 \mu m$ ,  $\rho = 1.7 \cdot 10^{-8} \Omega m$

Over method area =  $0.75 \cdot 10^{-3} \cdot 13 \cdot 10^{-6}$

$$R = \frac{\rho l}{A} = \frac{1.7 \cdot 10^{-8} \cdot 0.025}{9 \cdot 10^{-9}} = 0.047 \Omega$$

Resistor network

- small resistors can have a large resistance, but can only dissipate a modest amount of energy every second.
  - If the power generated in the resistor is too large, then a thermal fuse can occur.

Combining resistors

- series in which a resistor is followed by another.
  - Parallel, or when they're connected in a resistor, and one lead on close to one another.

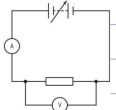


Figure 10

- In series have the same current in each component.
- the number of electron leaving the first component will be equal to the number of electron entering the second component.
- the resistors will add up.
- In parallel, the components will have the same pd across them.
- In parallel, when two resistors are added together, the cell will supply a greater current than if they were alone.
- In series, it will have to supply the sum of the separate currents.

	Currents ...	Potential differences ...
In series	...are the same	...add
In parallel	...add	...are the same

Resistors in series

- In series, there are 3 resistors,  $R_1, R_2, R_3$ .
- Have the same current in them, then the equivalent resistance of the resistors would be equivalent to:  $R_T = R_1 + R_2 + R_3$ .
- This means that the total resistance in series is adding the resistance of all the resistors.

Resistors in parallel

- The opposite will happen if the resistors are in parallel.
- In parallel, the resistors will all have the same pd.
- The total current will be given by:  $I_T = I_1 + I_2 + I_3$ .
- The total resistance will be given as:  $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$
- Eg calculation,  $R_1 = 10\Omega, R_2 = 10\Omega$
- $\frac{1}{R_T} = \frac{1}{10} + \frac{1}{10}$
- $\frac{1}{R_T} = \frac{2}{10}$  Reciprocal
- $R_T = 5\Omega$

More complicated networks

- When working out the total resistance of a network with series and parallel, the steps are:
- Combine the resistors in parallel into one equivalent resistor.
- Add resistors in parallel.
- Reciprocal

Potential divider

- This is a circuit which is usually used with sensors and to also produce variable potential differences.
- The most basic potential divider consist of two resistors ( $R_1$  &  $R_2$ ) in series with a power supply.
- This is to give a pd between 0 and the top of the power supply.

Figure 13(a)

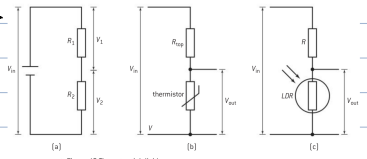


Figure 13 The potential divider

- The pd across a resistor will be given by the equations  $V_1 = \frac{R_1 V_{max}}{R_1 + R_2}$  and  $V_2 = \frac{R_2 V_{max}}{R_1 + R_2}$

Using a potential divider with sensors

- Typical sensor and variable circuit are figure 13(b) and (c).
- Figure 13(b) has a thermistor rather than a resistor.
- In winter, before, as the temp rises the resistance will fall.
- Reverse temp, in hot, thermistor resistance is high (compared to fixed resistor).

$V_{variable} = \frac{V_{in} R_{sensor}}{R_{sensor} + R_{fixed}}$  and  $V_{variable} = \frac{V_{in} R_{variable}}{R_{sensor} + R_{variable}}$


Although, if the resistance of the thermistor is considerably higher than the fixed resistor, then the potential for the thermistor will be approx that of the cell.

$R_{sensor} \gg R_{fixed} \rightarrow V_{sensor} \approx V_{in}$

- If the resistance of the thermistor ever to decrease, then that would mean that the potential across the fixed resistor would increase.
- The resistance of the fixed resistor is smaller than the resistance of the thermistor when it is at its maximum temperature.

- this is the same case with 10A, as the amount of potential incident increases, then the resistance will decrease.

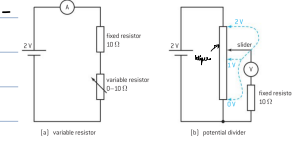Using potential divider to give a variable pd



- when the variable resistor is set to 0A (min value), then there is a pd of 2V across the resistor, and a current of 0.2Amps

- when the variable resistor is at 10A (max value), the total resistance will be 20A in the circuit, and a current of 0.1Amps

- meaning that only 1V is dropped across the variable resistor.

- therefore the range of the pd for the fixed resistor will be equal to 1-2V.

- the potential divider allows a greater range of pd to the test component than the variable resistor.

- the variable resistor can also be called a rheostat.

- in a potential divider one end of the wire will be connected to all and fixed resistor, and a second wire will be connected to the variable resistor and other end of the wire.

- the potential along the resistance usually depends on the position of the slider.

- the component under test will be connected to a secondary circuit between one terminal of the resistance usually and the slider on the variable resistor.

- when the slider is all the way to one end, then all 2V will be available to the resistor under test.

- when it's on the other end, the pd between the ends of the resistor is 0V.

Worked example

- 6V, 1000A = R, V max resistor = 1.5V → 0.50 = 6/1000

$$6 \cdot V = \frac{6 \cdot (R_{1000})}{(1000 + R_{1000})}$$

$$6 \cdot A_{1000} = \frac{6 \cdot A_{1000}}{2000 + 1000}$$

$$R_{1000} = 1000 \Omega$$

- as the temperature increases more charge carriers will be made available, and while this will also ensure that the atoms of the semiconductor will vibrate with greater amplitude and speed (leading to increase in resistance), the charge carrier effect will overcome the atoms' increased movement.

Energy effect equation

- the power dissipated in a component is given by P = IV.

- the energy converted in time is: E = IVt.

- If I or V isn't known then:  $E = IVt = I^2 R t = \frac{V^2}{R} t$

- this is the energy converted in different systems and components.

Worked example

- R = 250Ω, V = 10V → P =  $\frac{V^2}{R} = \frac{10^2}{250} = 0.4W$

$$P = \frac{V^2}{R} = \frac{100}{250} = 0.4W$$

$$I = \frac{V}{R} = \frac{10}{250} = 0.04A$$

R = 6.1A

Kirchoff's first and second laws

- if 10<sup>18</sup> charge carriers flow into a conductor, then 10<sup>18</sup> charge carriers will flow out.

- the figure shows that there are 3 incoming currents and two outgoing ones.



Figure 15 Kirchoff's first law

- therefore, the rule for the outgoing charge will be:  $I_1 + I_2 + I_3 = I_4 + I_5$

- this can be summarized to: for any junction  $\sum I = 0$ .

- this means that the currents can be positive, and the ones out as negative (physically speaking).

- can be stated in Kirchoff's first law, which is stated as: the sum of the currents flowing into a junction equals the sum of the currents flowing out of the junction.

- this is essentially the conservation of charge.

- Kirchoff second law is the conservation of energy.

- it applies to closed circuits.

- in a complete circuit loop the sum of the e.m.f.s in the loop is equal to the sum of the potential differences in the loop.

- symbols: for a closed loop  $\sum \mathcal{E} = \sum \mathcal{E}_R$ .



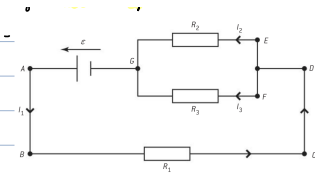


Figure 16 Kirchhoff's second law.

- In this loop there is one source of emf, and two resistors.
- therefore,  $\sum \text{emf of cell} = I_1 R_1 + I_2 R_2$  (this total job across the resistors).

Worked example

$\sum \text{emf} = IR$      $\sum \text{emf} = 3 \times 1$   
 $I = 0.18$      $I = 1.8 \times 10$   
 $I = 0.18$

$V = 50$ ,  $\frac{1}{R} = \frac{1}{4} + \frac{1}{6}$      $I = \frac{V}{R}$      $0.45 = I_1 + I_2$      $I_2 = 0.18 - I_1$      $I_2 = 0.18 - I_1$   
 $\frac{1}{R} = \frac{1}{4} + \frac{1}{6} = \frac{3}{12} + \frac{2}{12} = \frac{5}{12}$      $I_2 = 0.18 - I_1$      $I_2 = 0.18 - I_1$   
 $R = \frac{12}{5} = 2.4$      $V = I \left( \frac{12}{5} \right)$      $I_2 = 0.18 - I_1$      $I_2 = 0.18 - I_1$   
 $I = 0.18$      $V = 0.18 \times 2.4 = 0.432$      $I_2 = 0.18 - 0.18 = 0$      $I_2 = 0.18 - 0 = 0.18$

$R_1 = 350 \Omega$ ,  $R_2 = 500 \Omega$ ,  $V = 6.0 \text{ V}$      $R = \frac{350 \times 500}{350 + 500} = 200 \Omega$      $V = \frac{6.0 \times 200}{200} = 1.1 \text{ V}$   
 $V = \frac{6.0 \times 200}{700} = 1.71$      $R = 1.5 \Omega$ ,  $V = 3.0 \text{ V}$ ,  $I_{\text{avg}} = 30, 200 = 3$   
 $R = \frac{3}{300 \times 10^3} = 10 \mu\Omega$      $I = \frac{V}{R} = \frac{3}{10} = 0.3 \text{ A}$

5.3 Electric Cells

Equations:

- emf of a cell:  $\mathcal{E} = I(R+r)$

Cells

- avoid excess; ensure that the all drives in one direction.
- the distance along wires increases away from the negative terminal of the cell.
- they will be better in the positive terminal.
- the positive terminal of the cell will have a high potential compared to the negative terminal.
- as electrons appear to gain energy.

Primary and Secondary Cells

- primary cells are cells which are used until they are exhausted.
- this is because the original chemicals have completely reacted.
- e.g. Zn battery.
- secondary cells are cells which can be recharged.
- the chemical once exhausted can be converted to a charge, and the opposite reaction occurs.

The Leclanché cell is the original primary cell.

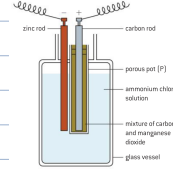


Figure 1 Leclanché cell and lead-acid accumulator.

- the zinc rod will be the negative terminal.
- the carbon rod will be the positive terminal.
- the lead acid battery in cars is a voltaic cell.

Capacity of cells

- the capacity of a cell is the quantity used to measure the ability of a cell to release charge.
- If a cell is discharged at a high rate, then it will run out in a short amount of time.
- the way that the capacity of a cell is written is in the amount of charge per the time it can supply it.
- e.g. 5 Ah for 20 hours = 40 amp-hours.
- this would mean that the cell would be able to provide 1 amp for 40 hours.

- The typical discharge curve would look like the following figure:

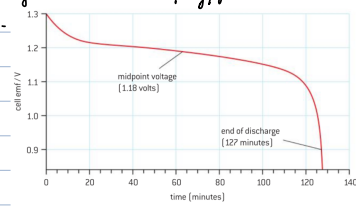


Figure 3 Typical discharge-time graph for a cell.

- Some important features for the graph are:

- The initial pd will be higher than the quoted one.
  - Although, it will fall down to the stated value in a short amount of time.
  - For most of the discharge time, the value of the pd will remain at the stated value.
  - After a point, there will be a gradual decrease in the pd.
  - As the cell approaches exhaustion, the pd will quickly decrease.
  - If the current is switched off, the pd will eventually go back up to its stated value.
  - When the current is back on, it will quickly fall back to the low value it was at again.
- The secondary battery's capacity will also decrease over time as it charges and discharges.

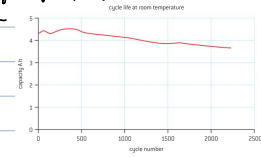


Figure 4 Cycle life of a rechargeable cell.

### - Internal resistance and e.m.f. of a cell

- Cells will have an internal resistance due to its material.

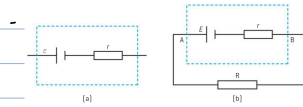


Figure 6

- Inside the dotted box is an "ideal" cell that has no resistance of its own.

- The 'r' box is the internal resistance.

- If the pd across the external resistor is  $V$ , then:  $\mathcal{E} = V + Ir$ .

- It also can be converted to:  $\mathcal{E} = IR + Ir$   
 $= I(R+r)$

- The terminal pd is the pd across an external resistor. The equation is:  $V = \mathcal{E} - Ir$ .

- The lost cell represents the energy required to drive the charge carriers through the cell.

- This causes the cell to warm up.

### - Worked example

-  $\mathcal{E} = 6.0V$ ,  $r = 2.5\Omega$ ,  $R = 7.5\Omega$  -  $V = IR = 4.5V$

$$\mathcal{E} = I(R+r)$$

$$I = 0.6A$$

-  $R = 6\Omega$ ,  $r = 1\Omega$ , when  $R = 3\Omega$ ,  $I = 1.5A$

$$\mathcal{E} = IR + Ir$$

$$\mathcal{E} = 6 \times 1.5$$

$$6 = 2 \times 1.5 + 1 \times 1.5$$

$$6 = 3 + 1.5$$

$$3 = 1.5$$

### - Power supplied by a cell

- The total power supplied by a non-ideal cell is given by:  $P = I^2(R+r)$ .

- The power delivered to the external resistance is:  $P = \frac{\mathcal{E}^2 R}{(R+r)^2}$ .

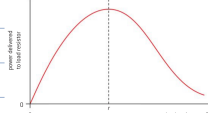


Figure 9 Power delivered to a resistor.

## 5.4 Magnetic effects of electric currents

### - Equations

- Force on a charge moving in a magnetic field:  $F = qvB \sin \theta$

- Force on a current-carrying conductor in a magnetic field:  $F = ILB \sin \theta$

### - Magnetic field patterns

- There is said to be a magnetic field at a point if a force acts on a magnetic pole at that point

- Magnetic field lines are similar to electric lines.

- Magnetic lines are drawn from the north to south pole.

- The strength of the field is shown by the density of the lines.


- Like electric lines, the closer the lines, the stronger the field.

- Field lines never cross.

- The field lines are an abut or parallel.
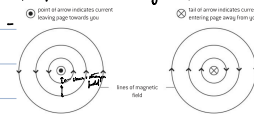
### - Magnetic field due to the current in conductors

- The magnetic field pattern due to a long straight wire is circular (or near circular):



- The right hand grip rule will show the current and magnetic field around a wire.


- The hand on the magnetic field, and the thumb is the conventional current.

- The strength of the magnetic field increases with:

- increasing the current.

- increasing the number of turns per unit length.

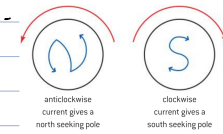
- adding an iron core on the inside of the wire.



▲ Figure 6 Right hand corkscrew rule and pole direction.

### - Forces on moving charges
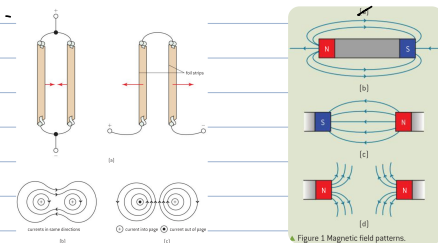
#### - Forces between two current-carrying wires



- when the currents are in the same direction, the wires move together due to the magnetic fields forces on the wires.

- when the currents are in the opposite direction, they'll repel one another.


- when the currents are in the same direction, the field lines from the poles combine to give a pattern in which the field lines loop around both poles.

- this can be seen in figure 1 c & d where the poles are opposite, the magnetic field will merge being the magnets together.


- On the other hand, when the currents are the opposite, they'll repel.
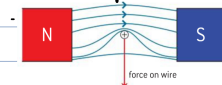
#### - Force between a bar magnet field and a current-carrying wire

- when a wire is placed in a magnetic field between two opposite poles, it will disrupt the field.



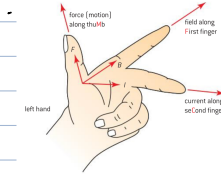- However, there will be a force applied on the wires.
- This is called a **catapult field**.
- This is used in speakers and motors, and is called the "motor effect".
- The movement of the wires is given by the left hand rule.



▲ Figure 9 Fleming's left-hand rule.

### - the motor effect

- The motor effect is the force and motion a current-carrying wire in the presence of a magnetic field experiences a force.


### - Worked example

- The wire will be attracted to wire P as they're both going in the same direction, causing the magnetic fields to merge, and attract, while the opposite will occur with wire R.

### - the magnitude of the magnetic force

- The force acting on the wire is proportional to:
  - the length  $l$  of the wire.
  - the current  $I$  in the wire.
- We define magnetic field strength as **force acting on a current element**  $\div$  **current  $\times$  length of element**.

- Written as:  $B = \frac{F}{IL}$

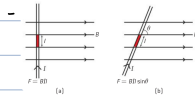

- If the element is at an angle, then sin can be used.

- The unit is **N/A**.

- The magnetic field of the Earth is  $10^{-4}$  T.

- The force equation changes to:  $F = BIL \sin \theta \rightarrow (40^\circ) F = BIL$ .

-  $\therefore \frac{F}{I} = B \rightarrow F = B \left( \frac{F}{I} \right) L \sin \theta \rightarrow F = BIL \sin \theta$

### - Worked example

-  $F = 0.2 \text{ N} \rightarrow F = 40 \text{ A}$

Force is 40 A